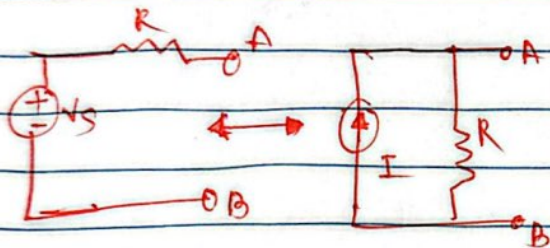



60

Find current across R_2
Using source transformation.




here, For $V_4 = R_4 \times I$
 $= 10\Omega \times 4A$
 $\therefore V_4 = 40V$

[transforming source]

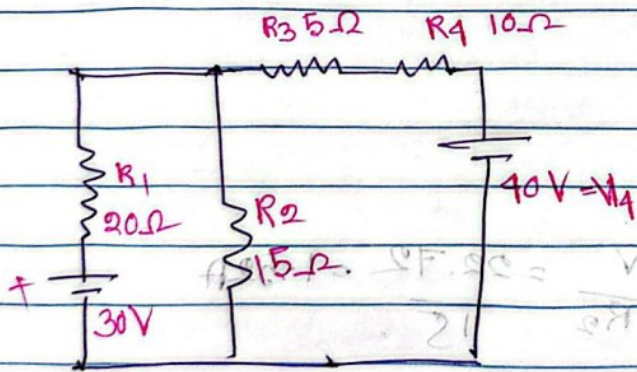

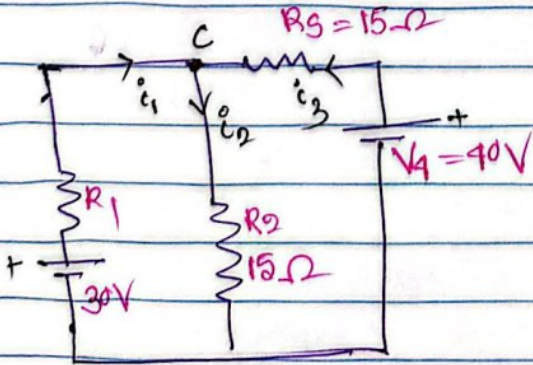here, R_3 & R_4 are series $\therefore R_5 = (R_3 + R_4) = (5 + 10) = 15\Omega$



applying KCL at C Node →

$$I_1 + I_3 - I_2 = 0$$

$$I_1 + I_3 = I_2$$

40

$$\frac{30-V}{20\Omega} + \frac{40-V}{15\Omega} = \frac{V}{15}$$

$$\frac{30-V}{20} + \frac{40-V}{15} - \frac{V}{15} = 0$$

$$\frac{30-V}{4} + \frac{40-V}{3} - \frac{V}{3} = 0$$

$$\frac{3(30-V) + 4(40-V) - 4V}{12} = 0$$

$$30 - 3V - 160 + 4V - 4V = 0$$

$$250 - 11V$$

$$11V = 250$$


$$\therefore V = 22.72V$$

$$\therefore \text{current across } R_2, I_2 = \frac{V}{R_2} = \frac{22.72}{15} = 1.52A$$


$$I_2 = 1.52A$$

10

Q2


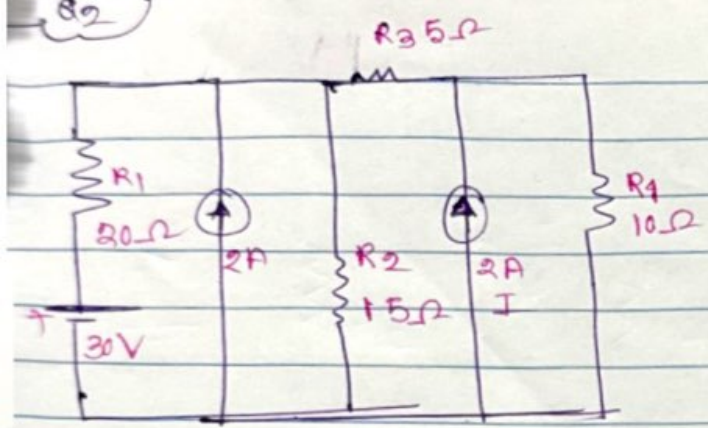


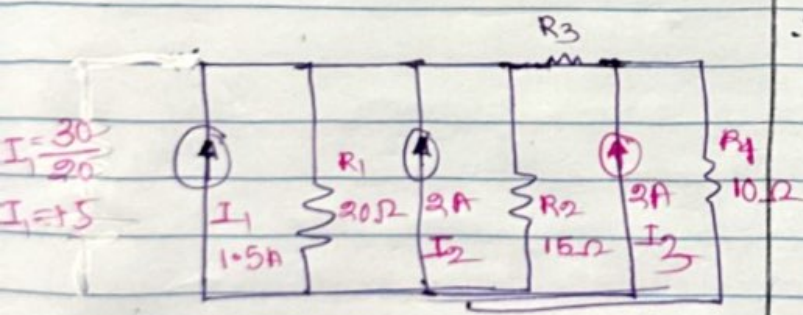Left side ~~current~~ ^{voltage} source will be transformed to a voltage source as below:-




here, R_1 & R_2 is parallel.
 $\therefore R_1 \parallel R_2$
 $\therefore R_p = (20^{-1} + 15^{-1})^{-1}$
 $\therefore R_p = 8.57 \Omega$

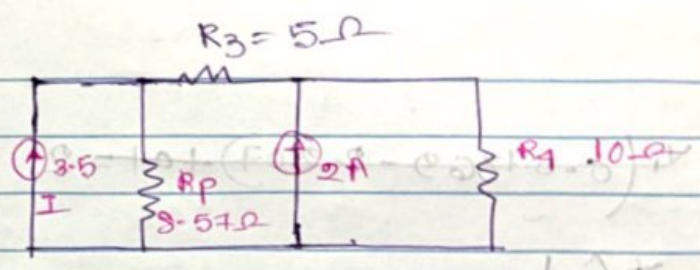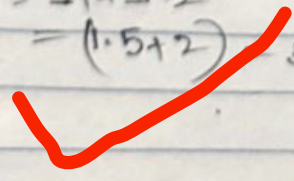
and,
 I_1 & I_2 are same direction
 So, $I = I_1 + I_2$
 $\therefore I = (1.5 + 2) = 3.5A$



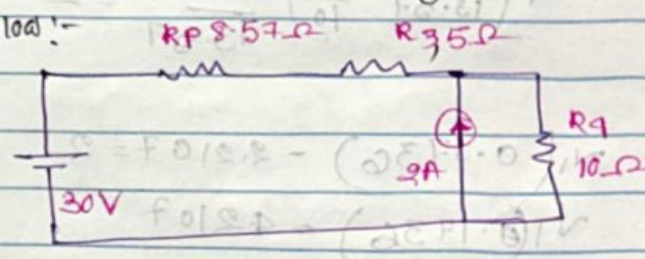Now, Left side current source will be transformed to a voltage source as below:-



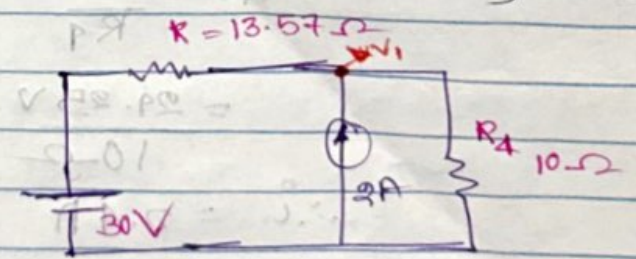$V = I \times R_p$
 $= (3.5A) \times (8.57 \Omega)$
 $\therefore V = 30V$
 $\therefore R_p$ & R_3 Series \rightarrow
 So, $R = R_p + R_3 = 13.57 \Omega$



Nodal analysis \rightarrow

$$\frac{V_1 - 30}{R_p} - 2 + \frac{V_1}{R_4}$$

$$= \frac{V_1 - 30}{13.57} - 2 + \frac{V_1}{10}$$

$$= \frac{V_1 - 30}{13.57} + \frac{V_1}{10} = 2$$

$$V_1 \left(\frac{1}{13.57} + \frac{1}{10} \right) - \frac{30}{13.57} = 2$$

$$V_1(0.07369 - 2.2107) + 0.1 = 2$$

$$V_1 \left(\frac{1}{13.57} + \frac{1}{10} \right) - \frac{30}{13.57} = 2$$

$$V_1(0.1736) - 2.2107 = 2$$

$$V_1(0.1736) = 4.2107$$

$$\therefore V_1 = \frac{4.2107}{0.1736}$$

$$\therefore V_1 = 24.25 \text{ V}$$

\therefore current across R_4 , $i = V_1$

$$= \frac{24.25 \text{ V}}{10 \Omega}$$

$$\therefore i = 2.4 \text{ A}$$

\therefore current across R_4 is 2.4 A

$$V + 0 = 08.1 \text{ V}$$

$$V + 0 = 08.1 \text{ V}$$


$$0 = V + 08.1 \text{ V}$$

$$0 = V + 08.1 \text{ V}$$

$$0 = \frac{1}{0.1} + \left(\frac{0.2}{13.57} + \frac{1}{10} \right) V$$

10

✓

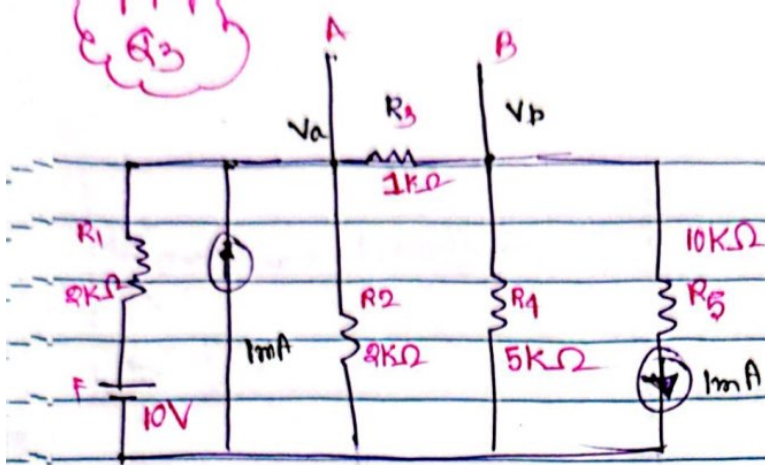

What is V_{AB} using thevenin's Theorem.

$$V_{Th} = V_A - V_B = V_{AB}$$

KCL at node V_A ,

$$\frac{10 - V_A}{8k\Omega} + 1mA - \frac{V_A}{2k\Omega} + \frac{V_B - V_A}{1k\Omega} = 0$$

$$10 - V_A + 2 - V_A + 2V_B - 2V_A = 0$$

$$2V_B - 4V_A = -12$$

$$V_B - 2V_A = -6$$

$$2V_A - V_B = 6 \quad (1)$$

applying KCL at node V_B ,

$$\frac{V_A - V_B}{1k\Omega} - \frac{V_B}{5k\Omega} - 1mA = 0$$

$$5V_A - 5V_B - V_B - 5 = 0$$

$$5V_A - 6V_B = 5 \quad (2)$$

$$(1) \times 6 - (2) \times 6 = (2) \times 6 - 5$$

$$(1) \times 6 - (2) \times 6 = 2 \rightarrow$$


$$12V_A - 6V_B - 5V_A + 6V_B = 36 - 5$$

$$7V_A = 31$$

$$\therefore V_A = 31/7 = 4.428V$$

$$\begin{aligned}
 V_D &= 2V_A - 6 \\
 &= (2 \times 4.428) - 6 \\
 &= 8.856 - 6 \\
 &= 2.857V
 \end{aligned}$$
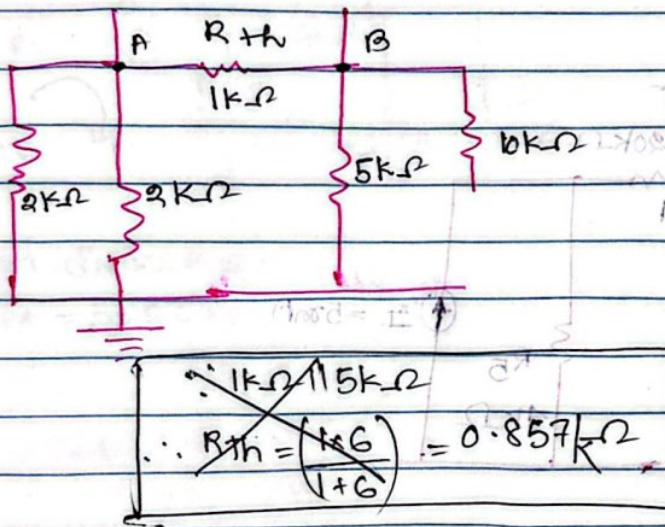
$$\begin{aligned}
 \therefore V_{Th} &= V_A - V_D \\
 &= 4.428 - 2.857 \\
 &= 1.57V
 \end{aligned}$$




$$\therefore R_{Th} = \left(\frac{1 \times 6}{1+6} \right) = 0.857k\Omega$$

$$\begin{aligned}
 R_{Total} &= (2k\Omega \parallel 2k\Omega) + 5 \\
 &= \left(\frac{2 \times 2}{2+2} \right) + 5k\Omega \\
 &= (1k\Omega) + 5k\Omega
 \end{aligned}$$

$$\therefore R_{Total} = 6k\Omega$$

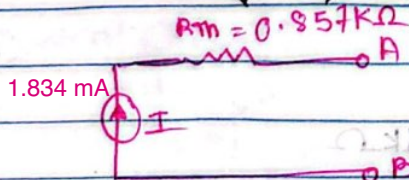
$$\therefore R_{Th} = \left(\frac{1 \times 6}{1+6} \right) = \frac{6}{7} = 0.857k\Omega$$



$$\text{Norton Current} = \frac{V_{Th}}{R_{Th}} = \frac{1.572V}{0.857k\Omega}$$


$$\therefore I = 1.834mA$$

Q1

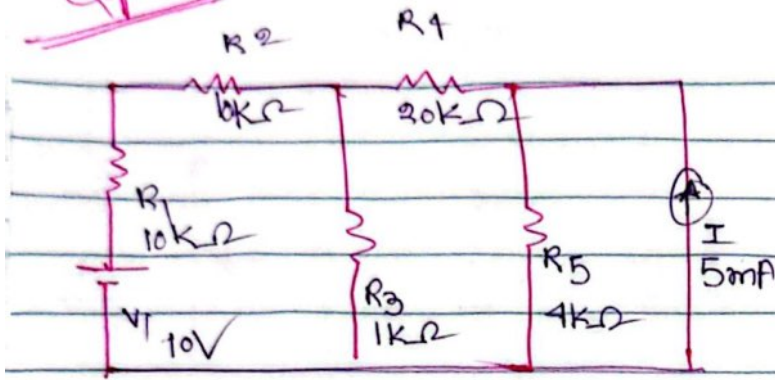


what is current of R_2 $I_{R2} = ?$
Using Thevenin's Theorem.

Thevenin's Voltage R_{th} :-

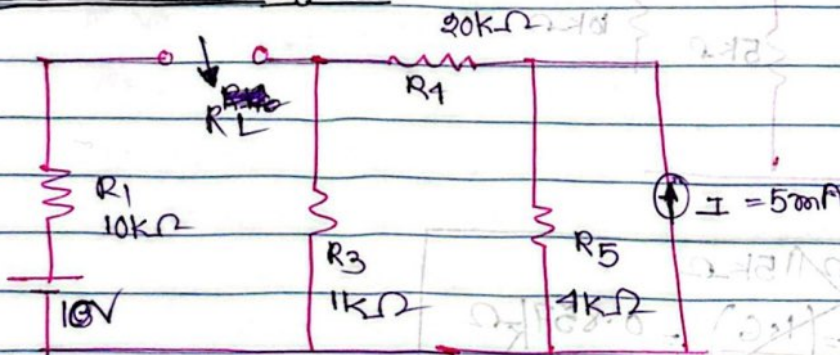

Calculating R_{th} , voltage source will be short circuit and current source will be open circuit.

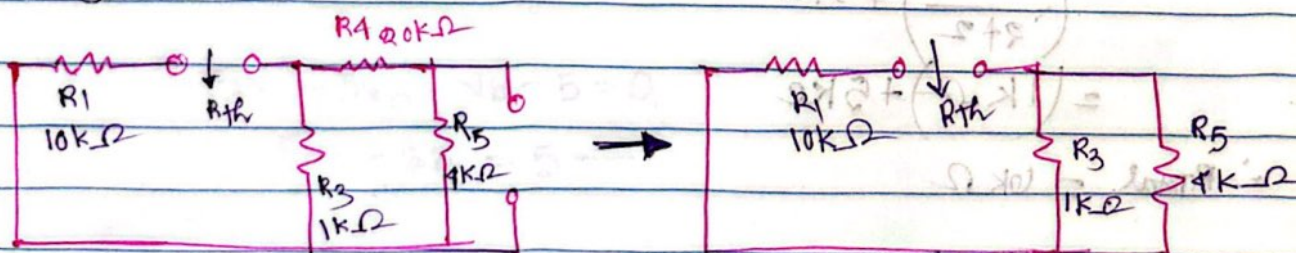So the circuit will be like this \rightarrow



here, we can see, $(R_4 + R_5) \parallel R_3$

$$R_{th} = R_1 + (R_4 + R_5) \parallel R_3$$

$$= 10k\Omega + (20k\Omega + 4k\Omega) \parallel 1k\Omega$$

$$= (24k\Omega) \parallel 1k\Omega + R_1$$

$$= R_1 + \left(\frac{24k\Omega \times 1k\Omega}{24k\Omega + 1k\Omega} \right)$$


$$R_1 + 960 \Omega$$

$$= (10000 + 960) \Omega$$

$$= 10960 \Omega$$

$$\therefore R_{th} = 10960 \Omega \text{ or } 10.96 \text{ K}\Omega$$

Thevenin Voltage (V_{th}):

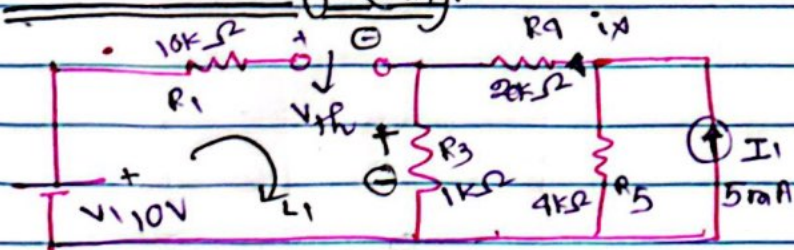

Current divider Rule

$$I_x = 5\text{mA} \times \left(\frac{R_5}{R_3 + R_4 + R_5} \right)$$

$$= 5\text{mA} \times \left(\frac{4\text{K}\Omega}{1\text{K}\Omega + 2\text{K}\Omega + 4\text{K}\Omega} \right)$$

$$= 5\text{mA} \times 0.10\text{K}\Omega$$

$$\therefore I_x = 0.8\text{mA}$$

Applying KVL at Loop 1


$$10\text{V} - V_{th} - R_3 i_x = 0$$

$$10 - V_{th} - (1\text{K}\Omega \times 0.8\text{mA}) = 0$$

$$10 - (1 \times 0.8) = V_{th}$$


$$\therefore V_{th} = 9.2\text{V}$$

Equivalent Circuit:

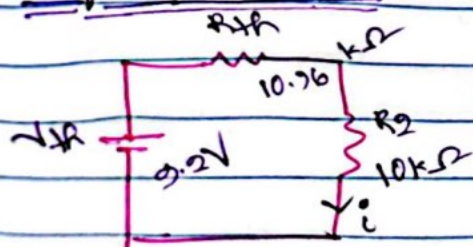

$$\therefore i = \frac{V_{th}}{R_{th}} = \frac{9.2}{(10.96\text{K}\Omega + 10\text{K}\Omega)} = 0.4389\text{mA}$$

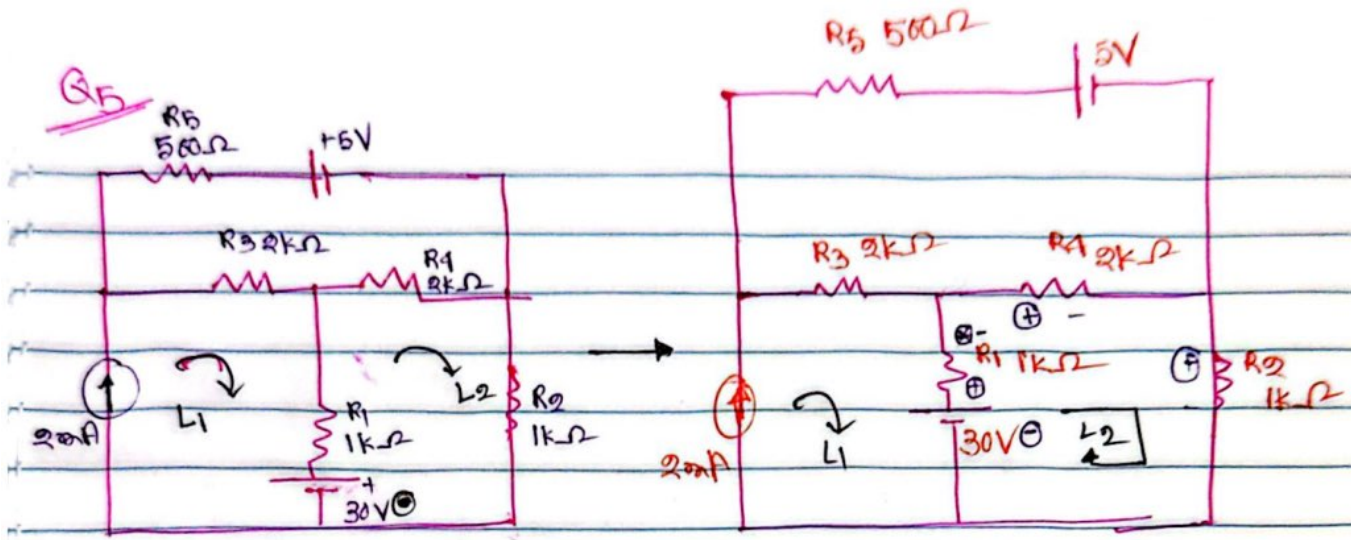\therefore current across R_2 is 0.4389mA .



Using mesh analysis, find V_0 across R_2 .

Loop 1 $\rightarrow i_1 = 2\text{mA} = 0.002\text{A}$.

Loop 2 applying KVL \rightarrow

$$-30 + R_1(I_2 - I_1) + R_4(I_2 - I_3) + I_2 R_2 = 0$$

$$-30 + 1\text{k}\Omega(I_2 - 0.002) + 2\text{k}\Omega(I_2 - I_3) + 1\text{k}\Omega I_2 = 0$$

$$-30 + 1000 I_2 - 2000 I_3 + 2000 I_2 - 2000 I_3 + 1000 I_2 = 0$$

$$4000 I_2 - 2000 I_3 = 30 \quad \text{--- (i)}$$

Loop 3 applying KVL \rightarrow

$$5 + R_4(I_3 - I_2) + R_3(I_3 - I_1) + R_5 I_3 = 0$$

$$5 + 2000 I_3 - 2000 I_2 + 2000 I_3 - 2000 I_1 + 500 I_3 = 0$$

$$-2000 I_2 + 4500 I_3 + 1 = 0 \quad \text{--- (ii)}$$

$$-2000 I_2 + 4500 I_3 = -1 \quad \text{--- (ii)}$$

Solving (i) & (ii) $\rightarrow i_2 = 0.0101\text{A}$.

$$i_3 = 0.004285\text{A}$$


$$\therefore V_0 \text{ across } R_2 = i_2 \times R_2$$

$$= (0.0101\text{A}) \times (1\text{k}\Omega)$$

$$= 10.1428\text{V}$$

$$\therefore V_0 \text{ across } R_2 \text{ is } 10.1428\text{V}$$

Q6

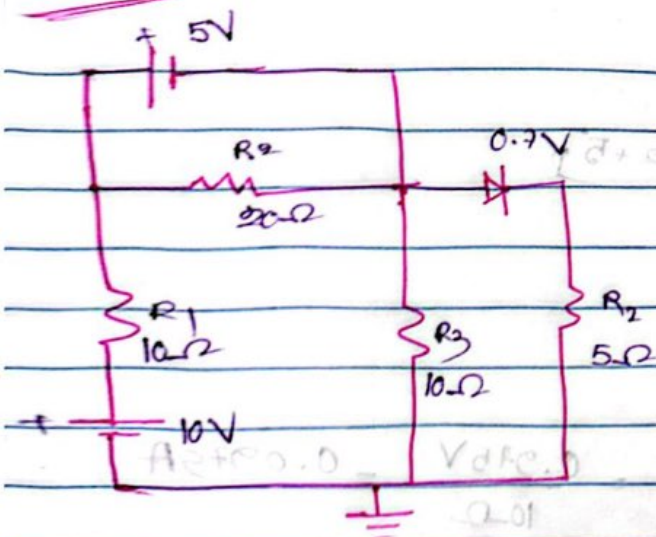


$$8.00 = 2V_2 + 2V_2 + 2V_2$$

$$8.00 = 6V_2$$

$$V_2 = 1.33V$$

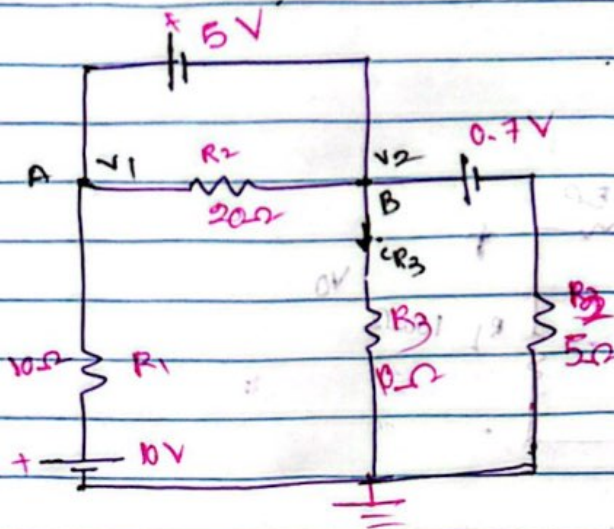the built in voltage of diode is 0.7 V. So, replacing the diode with 0.7 V of battery.



Consider the Node voltage V_1, V_2 in the above circuit.

$$\therefore V_1 - 5 = V_2$$

$$\therefore V_1 = V_2 + 5 \quad \text{--- (i)}$$

Applying Nodal Analysis \rightarrow

$$\frac{V_1 - 10}{10} + \frac{V_1 - V_2}{20} + \frac{V_2 - 0}{10} + \frac{V_2 - 0.7}{5} = 0$$

$$\frac{V_1 - 10}{10} + \frac{V_1 - V_2}{20} + \frac{V_2}{10} + \frac{V_2 - 0.7}{5} = 0$$

Multiply whole equation by 20,

$$2(V_1 - 10) + V_1 - V_2 + 2V_2 + 4(V_2 - 0.7) = 0$$

$$2V_1 - 20 + V_1 - V_2 + 2V_2 + 4V_2 - 2.8 = 0$$


$$3V_1 + 5V_2 = 22.8 \quad \text{--- (2)}$$

$$3(V_2 + 5) + 5V_2 = 22.8 \quad \text{[As } V_1 = V_2 + 5]$$

$$3V_2 + 15 + 5V_2 = 22.8$$

$$8V_2 = 7.8$$



$$\therefore V_2 = 0.975V$$

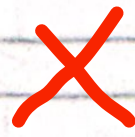

Using Ohm's law,

$$\text{the current through } R_3, i_{R_3} = \frac{V_2}{R_3} = \frac{0.975V}{10\Omega} = 0.0975A$$

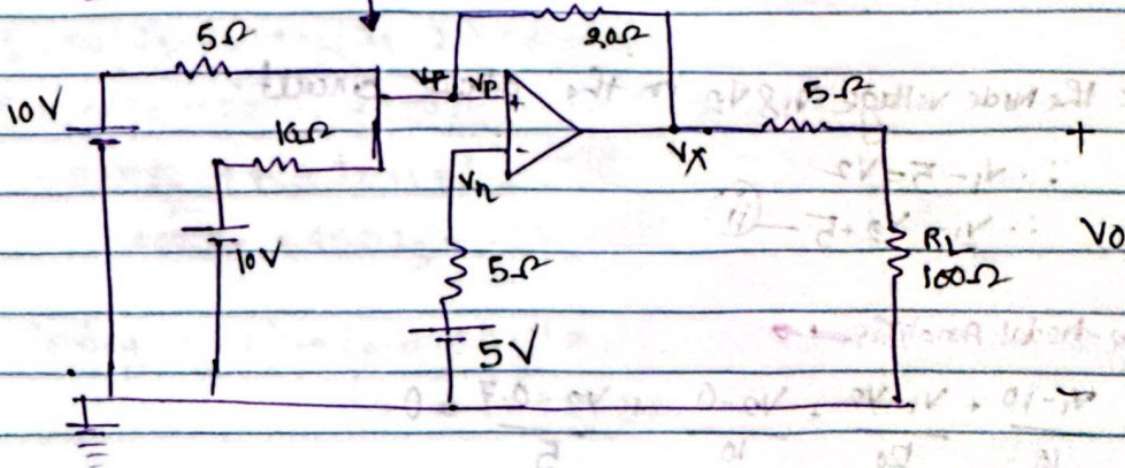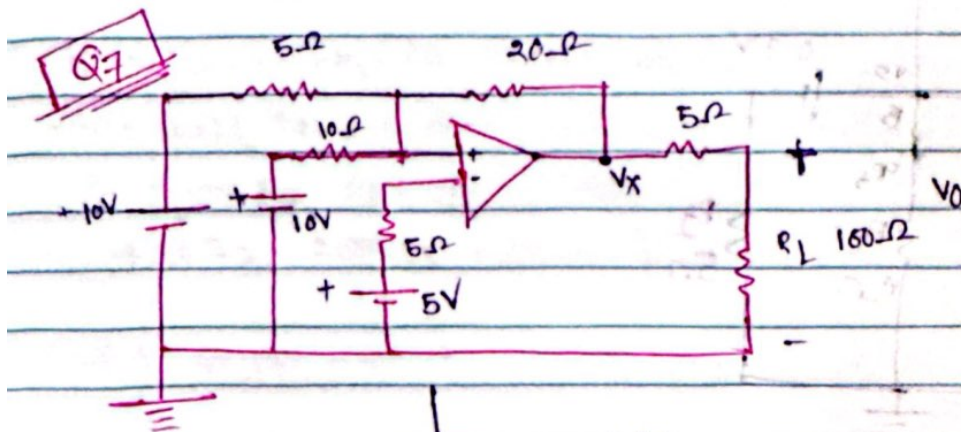\therefore current of R_3 resistor is $0.00975A$ or $9.75mA$



here V_p & V_n are the voltages of inverting terminal & Non-inverting terminal according to the figure.

$$\text{So, } V_p = V_n$$

$$\therefore V_n = 5V + 2V \cdot 1V = (5 + 2)V$$

$$\therefore V_p = 5V + 1V + 0.5 \cdot 1V = 6.5V$$

applying KCL at $V_p \rightarrow$

$$\frac{V_p - 10}{5} + \frac{V_p - 10}{10} + \frac{V_p - V_x}{20} = 0$$

$$\frac{5 - 10}{5} + \frac{5 - 10}{10} + \frac{5 - V_x}{20} = 0$$

$$-1 + \left(-\frac{1}{2}\right) + \frac{5 - V_x}{20} = 0$$

$$-\frac{3}{2} + \frac{5 - V_x}{20} = 0$$

$$\frac{5 - V_x}{20} = \frac{3}{2}$$

$$2(5 - V_x) = 60$$

$$5 - V_x = 30$$

$$V_x = -25V$$

By Voltage Divider Rule, the voltage across R_L is given by,

$$V_0 = \left(\frac{R_L}{5 + R_L} \right) \times V_x$$

$$= \frac{(100) \times -25}{(5 + 100)}$$

$$V_0 = \frac{-2500}{105}$$

$$\therefore V_0 = -23.8095V$$

10

